

## 21. HALF ADDER

**EXP.NO: 21**

**AIM:** To design and implement the two bit half adder using Logisim simulator.

### PROCEDURE:


- 1) Pick and place the necessary gates.
- 2) Insert 2 inputs into the canvas.
- 3) Connect the inputs to the XOR gate and AND gate.
- 4) Insert 2 outputs into the canvas.
- 5) Make the connections using the connecting wires.
- 6) Verify the truth table.

### TRUTH TABLE:


Truth Table			
Input		Output	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = A \text{ XOR } B \quad C = A \text{ AND } B$$


Logical Diagram:

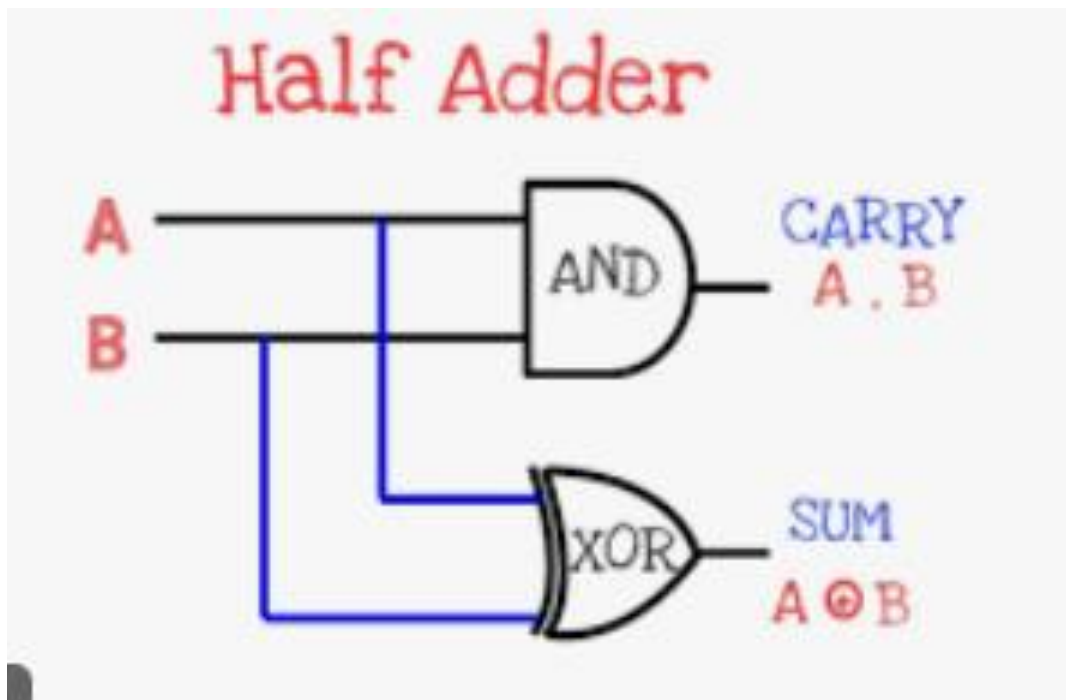


Half Adder using NAND Gates:

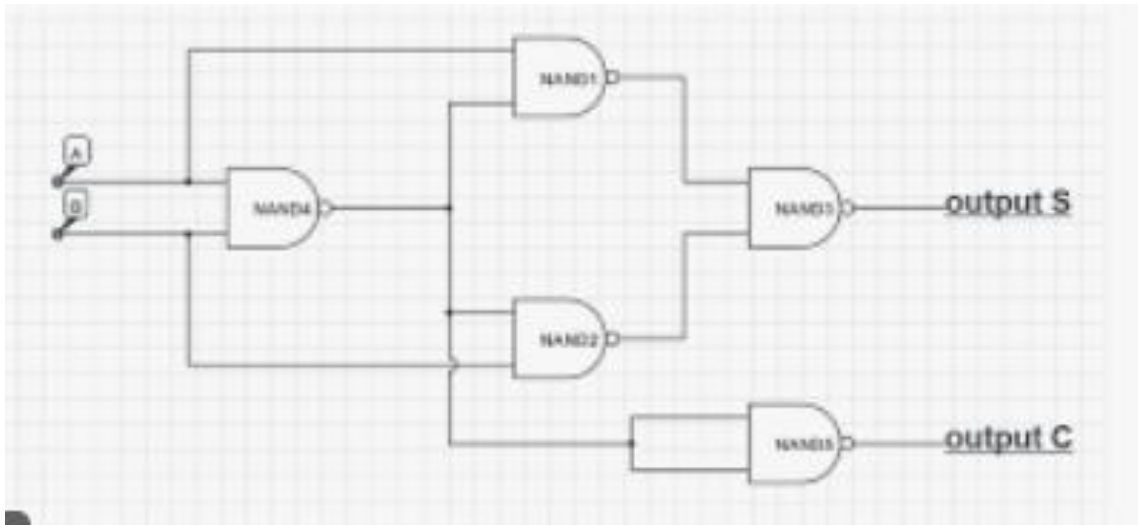

Half Adder using NOR Gates:

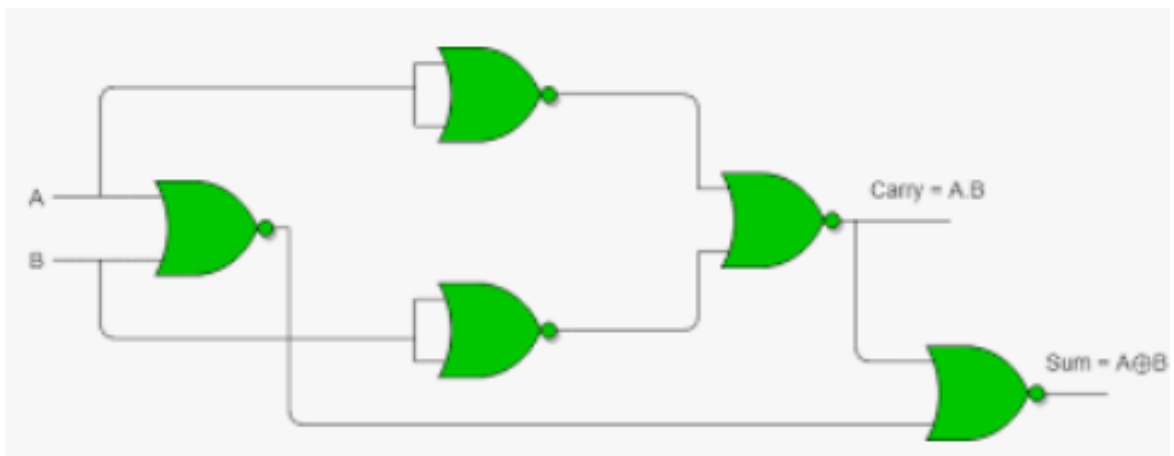

## OUTPUT

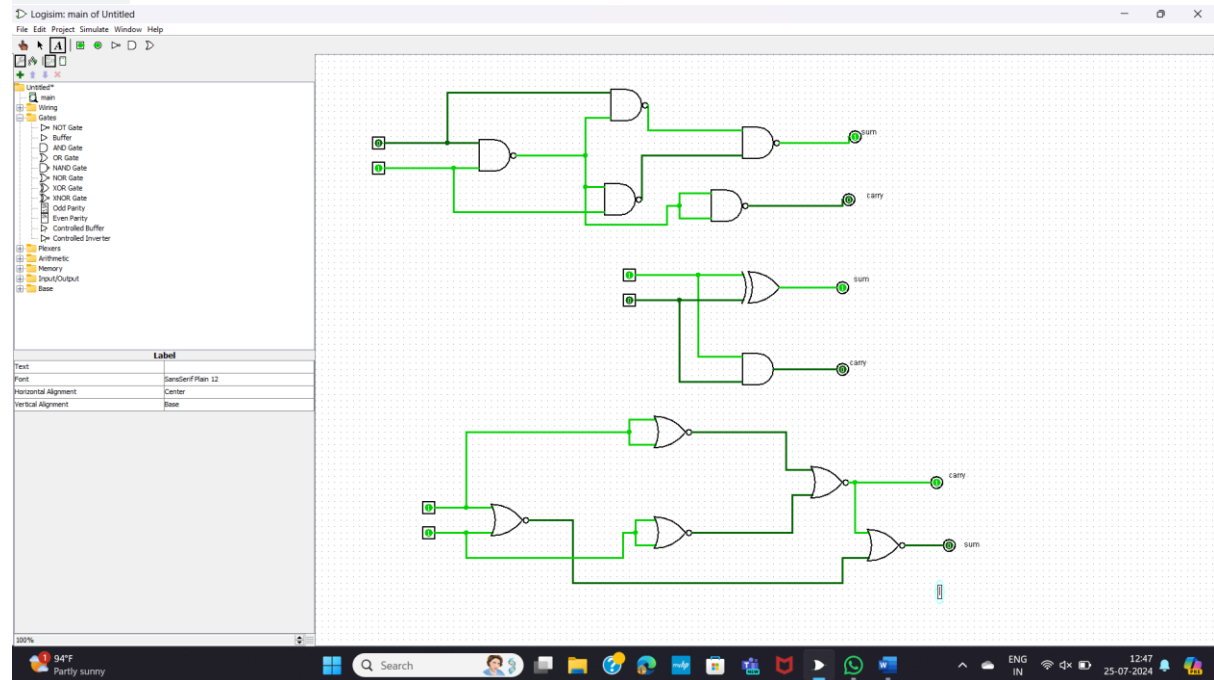

**RESULT:** Thus 2-bit half adder has been designed and implemented successfully using logisim simulator.